

**2020**  
**PHYSICS – GENERAL**  
**Practical Paper**  
**PAPER: IVB**  
**Full Marks: 50**

*Candidates are required to give their answers in their own words as far as practicable.*  
*The figures in the margin indicate full marks.*

**Module I (Computer lab)**

**Marks-25**

*Answer **any one** from the following questions.*

1. Write a program in C or Fortran to sort the following numbers in ascending and descending order. Also find the smallest and largest number.

[43, 67, 32, 87, 21, 9, 98, 67]

2. Write a program in C or Fortran to find the mean, median and mode of the following numbers-

[33, 55, 77, 22, 99, 11, 66, 44, 88]

3. Write a program in C or Fortran to find the real or imaginary roots of the following quadratic equation-

$$7x^2 - 5x + 9 = 0$$

4. Write a program in C or Fortran to add and subtract following two 3×3 matrices-

$$\begin{bmatrix} 3 & 5 & -2 \\ 7 & -3 & 6 \\ -9 & 6 & 3 \end{bmatrix} \text{ and } \begin{bmatrix} -4 & 5 & 7 \\ 2 & -8 & 9 \\ 6 & 3 & -7 \end{bmatrix}$$

**Please Turn Over**

## Module II

### Marks-25

Answer **any one** from the following questions.

5. To use OP AMP as non-inverting amplifier –

- (a) Draw the circuit diagram.
- (b) Calculate  $V_0$ , when  $V_i = 0.1 \text{ V}, 0.2 \text{ V}, 0.4 \text{ V}, 0.5 \text{ V}, 0.7 \text{ V}$ .  
[Given,  $R_1 = 1 \text{ k}\Omega$ ,  $R_2 = 10 \text{ k}\Omega$ ]
- (c) Calculate gain in each case.
- (d) Draw a graph  $V_0$  against  $V_i$ .
- (e) What are the characteristics of an ideal OP AMP ? (5+5+5+8+2)

6. To use OP AMP as inverting amplifier –

- (a) Draw the circuit diagram.
- (b) Calculate  $V_0$ , when  $V_i = 0.1 \text{ V}, 0.3 \text{ V}, 0.4 \text{ V}, 0.6 \text{ V}, 0.8 \text{ V}$ .  
[Given,  $R_1 = 1 \text{ k}\Omega$ ,  $R_2 = 5 \text{ k}\Omega$ ]
- (c) Calculate gain in each case.
- (d) Draw a graph  $V_0$  against  $V_i$ .
- (e) Mention some of the uses of OP AMP ? (5+5+5+8+2)

7. To use OP AMP as differential amplifier –

- (a) Draw the circuit diagram.
- (b) Calculate  $V_0$ , when  $V_1 = 0.1 \text{ V}, V_2 = 0.2 \text{ V}$ ; when  $V_1 = 0.2 \text{ V}, V_2 = 0.5 \text{ V}$ ; when  $V_1 = 0.3 \text{ V}, V_2 = 0.7 \text{ V}$ ; when  $V_1 = 0.4 \text{ V}, V_2 = 0.9 \text{ V}$ ; and when  $V_1 = 0.4 \text{ V}, V_2 = 1 \text{ V}$ .  
[Given,  $R_1 = 1 \text{ k}\Omega$ ,  $R_2 = 10 \text{ k}\Omega$ ]
- (c) Calculate gain in each case.
- (d) Draw a graph  $V_0$  against  $V_i$ .
- (e) What do you understand by virtual ground of an OP AMP ? (5+5+5+8+2)

**Please Turn Over**

8. To use OP AMP as three input adder –

- Draw the circuit diagram.
- Calculate  $V_0$ , when  $V_1 = 0.1$  V,  $V_2 = 0.2$  V,  $V_3 = 0.3$  V ; when  $V_1 = 0.2$  V,  $V_2 = 0.3$  V,  $V_3 = 0.5$  V ; when  $V_1 = 0.3$  V,  $V_2 = 0.5$  V,  $V_3 = 0.6$  V ; and when  $V_1 = 0.4$  V,  $V_2 = 0.6$  V,  $V_3 = 0.8$  V . [Given,  $R_1 = R_2 = R_3 = 1$  k $\Omega$  ,  $R_f = 5$  k $\Omega$ ]
- Draw a graph  $V_0$  against  $V_i$  .
- Why is an OP AMP usually used with a negative feedback ?
- What is offset null adjustment of an OP AMP ? (5+8+8+2+2)

9. To convert a given ammeter into a voltmeter –

- Draw the circuit diagram.
- Write down the working formula.
- Find out the multiplier resistance ( $R_s$ ), for current ( $I_m$ ) = 100  $\mu$ A , voltage (V) = 1 V and internal resistance ( $R_m$ ) of the ammeter,  $R_m = 1$  k $\Omega$  .
- Using following data draw a calibration graph of prepared voltmeter reading ( $V_{prep}$ ) against standard voltmeter reading ( $V_{std}$ ) , for conversion of an ammeter of range (0–100)  $\mu$ A into a voltmeter of range (0–1) V.

$V_{prep}$ (Volt)	0.1	0.2	0.3	0.5	0.7
$V_{std}$ (Volt)	0.15	0.25	0.35	0.55	0.75

(5+5+5+10)

10. To convert a given voltmeter into an ammeter –

- Draw the circuit diagram.
- Write down the working formula.
- Find out the shunt resistance ( $R_{sh}$ ), where current for full deflection of voltmeter ( $I_m$ ) = 100  $\mu$ A ,  $I = 100$  mA , voltage (V) = 1 V and internal resistance ( $R_m$ ) of the ammeter,  $R_m = 10$  k $\Omega$  .
- Using following data draw a calibration graph of prepared ammeter reading ( $I_{prep}$ ) against standard ammeter reading ( $I_{std}$ ) , for conversion of a voltmeter of range (0–1) V to an ammeter of range (0–100) mA.

$I_{prep}$ (mA)	10	20	40	60	80
$I_{std}$ (mA)	15	25	45	65	85

(5+5+5+10)